

Seat No. _____

QP-3258

Total No. of Pages : 3

OCT_NOV_2024 WINTER EXAMINATION

12329 Bachelor of Computer Application(BCA) NEP 2.0

Sub. Name: Computer Architecture

Sub. Code: 109808

Day and Date: FEBRUARY ,17-02-2025

Total Marks: 60

Time: 10:30 AM To 12:30 PM

Instructions: 1. Figures to the right indicate full marks

Special Inst.: 1) Que.No.1 and Que. No. 7 are compulsory.

2) Attempt any THREE questions from Que. No.2 to Que. No. 6.

Q1) Solve following MCQ.

[10]

- i. Convert binary to octal: (110110001010)₂
 - A. (5512)₈
 - B. (6612)₈
 - C. (4532)₈
 - D. (4130)₈
- ii. The decimal equivalent of the binary number (1011.011)₂ is
 - A. (11.175)₁₀
 - B. (11.375)₁₀
 - C. (10.123)₁₀
 - D. (9.23)₁₀
- iii. The gates required to build a half adder are ____
 - A. EX_OR Gate And AND Gate
 - B. EX-OR Gate And OR Gate
 - C. EX-NOR Gate And AND Gate
 - D. EX-OR Gate And NOR Gate
- iv. 2's complement of binary number 0101 is
 - A. 1101
 - B. 1111
 - C. 1011
 - D. 1110
- v. In boolean algebra, the OR operation is performed by which properties?
 - A. Associative Properties
 - B. Commutative Properties
 - C. Distributive Properties
 - D. All Of Above
- vi. The gates required to build a half adder are ____

- A. EX-OR gate and NOR gate
 B. EX-OR gate and OR gate
 C. EX-OR gate and AND gate
 D. EX-NOR gate and AND gate

vii. Which of the examples below expresses the commutative law of multiplication?

- A. $A + B = B + A$
 B. $A \cdot B = B + A$
 C. $A \cdot (B \cdot C) = (A \cdot B) \cdot C$
 D. $A \cdot B = B \cdot A$

viii. Why do we use gray codes?

- A. To count the no of bits changes
 B. To rotate a shaft
 C. Error correction
 D. Error Detection

ix. Whose operations are more faster among the following?

- A. Combinational circuits
 B. Sequential circuits
 C. Latches
 D. Flip-flops

x. Which memory has largest storage capacity among all?

- A. Auxiliary memory
 B. RAM
 C. Associative memory
 D. Cache memory

Q2) What are logic gates? Explain different logic gates with their truth tables and [10]
 diagram.

Q3) What is Flip flops? Explain SR and D flip flop with necessary diagrams. [10]

Q4) What is Karnaugh map (K' Map)? Why it is used? Explain with an example. [10]

Q5) Explain Binary, Octal and Hexadecimal number system and with suitable examples [10]
 number conversion from Decimal to Binary, Octal and Hexadecimal?

Q6) Describe in brief Memory Hierarchy of Memory organization in detail. [10]

Q7) Write short note (Any Four out of Six) [20]

a. SOP and POS

b. Decoders and Encoder

c. Half Adder and Full Adder

QP-3258

[5]

d. Program Counter and Accumulator registers

[5]

e. DeMorgan Laws

[5]

f. Shift registers

[5]

End Of Question Paper

Important Note for Chief Exam Officer / SRPD Coordinator / Sr Supervisor/ Student -

This Question Paper may be distributed for following Subjects as common code.

सदरची प्रश्नपत्रिका खालील विषयांकरिता वितरित करता येईल.

1] (12329) Bachelor Of Computer Application (NEP2.0) (109808) Computer Architecture Part 1 SEM 1